



Theoretisches Aufgabenblatt 2

Abgabetermin: 03 - 05.11.2014

1. Suppose there are two boolean functions P and Q :

$$P = (X + \bar{Y})(Y \oplus Z)$$

$$Q = \bar{Y}Z + XY\bar{Z}.$$

- Design a network of gates, consisting solely of AND, OR and NOT-Gates realizing P and Q out of the inputs X , Y und Z !
 - Are the boolean functions P and Q equivalent?
 - Discuss speed(latency) and costs of the subnets for P and Q !
2. Derive from the truth table of the boolean function $Y(a, b, c)$ the „min“ and „max“ terms. Use these to derive the disjunctive normal form as well as the conjunctive normal form. Simplify the resulting formulas and show their equivalenz.

a	b	c	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

3. To develop a drain control system a network of gates shall be developed. the drain system consists of four individual pipes.
- Two incoming drains have a capacity of $30 \frac{l}{min}$
 - One incoming drain has a capacity of $60 \frac{l}{min}$
 - One overflow drain is opened only if the incoming capacity is bigger then $70 \frac{l}{min}$

Model the system as boolean Input- and Output-Variables. Derive a helper variable y depending on the incoming drains x_1, x_2, x_3 . Develop the final boolean function $y = f(x_1, x_2, x_3)$.

4. Implement a 4:1 Multiplexer with 4 Inputs e_0, e_1, e_2 und e_3 controlled by s_0, s_1 towards towards the output a . Create a
 - a) Thruth Table,
 - b) Gate-network consisting solely of NAND-Gates.
 - c) ein Schaltbild aus 2:1 Multiplexern.

5. Mimic a traffic light using a decoder. Use the two input signals x_0 und x_1 to control three output values $Y = \{y_0, y_1, y_2\}$ to indicate four states „red“, „yellow-red“, ‘yellow‘ und „green“.
 - a) Create a thruth table for this functionality.
 - b) Derive the boolean function $Y = \{y_0, y_1, y_2\}$.