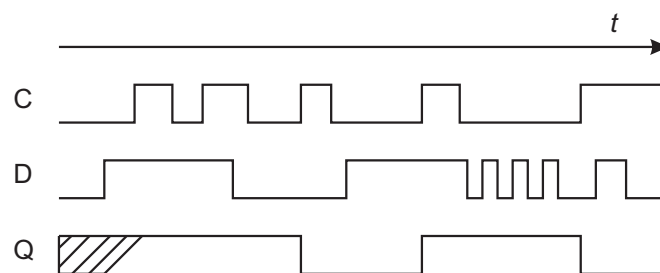





## Theoretisches Aufgabenblatt 4

Abgabetermin: 15.11.-17.11.2014

1. Which type of clocking is used in the D-Flip-Flop? The timing diagram of the Flip-Flop's signal is shown below:



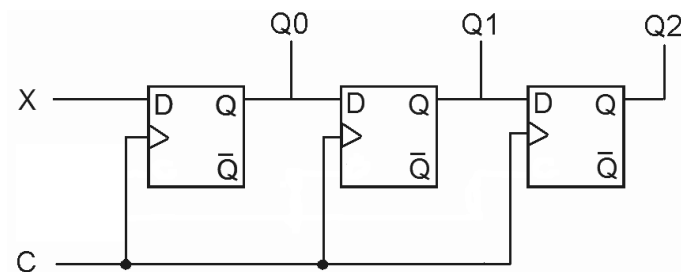2. Describe the difference between Mealy- and Moore-Automatas?
3. Construct a table of state transitions of the following logic circuit.



Which mathematical operation is implemented in this circuit?

4. Construct an automaton implementing a switchable 2-bit counter. On input  $E = 0$  the counter will count upwards, on  $E = 1$  it shall count downwards.
  - a) Construct the state graph based on Figure 1
  - b) Complete the binary state transition table (Tabelle 1).
  - c) The automaton shall be implemented using D-Flip-Flops. Infer the boolean function from the state transition table.
  - d) Simplify the boolean function.

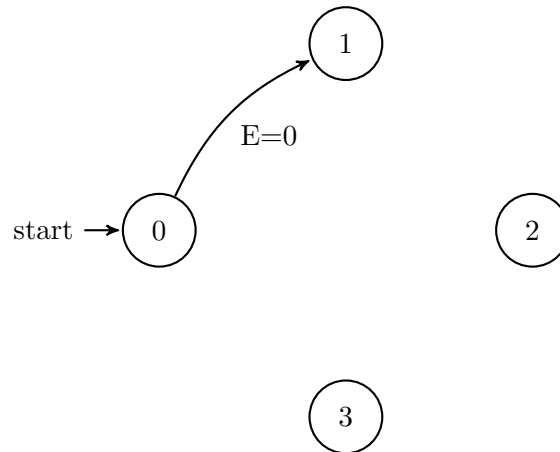


Abbildung 1: State transition graph

Tabelle 1: Binary state transition table

Input x	current State		next State	
	F	G	F'	G'
0				
1				
0				
1				
0				
1				
0				
1				

5. Construct an automaton implementing the control of a traffic light. The automaton uses one input  $e_0$  as well as three outputs  $y_0, y_1, y_2$  representing the three traffic light colors green, yellow and red. Provide reasons, why you chose a Mealey- or Moore-Automaton! Use the provided truth tables (1(a) and 1(b)). Welche Bausteine könnten

(a) Output table

$x_1$	$x_0$	Y	$y_2$	$y_1$	$y_0$
0	0	Rot	1	0	0
0	1	Rot-Gelb	1	1	0
1	0	Grün	0	0	1
1	1	Gelb	0	1	0

(b) Zustandsübergangstabelle

$e_0$	$x_1$	$x_0$	$x'_1$	$x'_0$
0	x	x	$x_1$	$x_0$
1	0	0	0	1
1	0	1	1	0
1	1	0	1	1
1	1	1	0	0

für die Umsetzung des Automaten verwendet werden?